

CS 6601 Secure Data Analysis - Fall 2017

Homework 1

Adam Bowers

Sammie Bush

Dalton Cole

September 21, 2017

Problem 1 Show how to construct the garbled circuit.

The normal circuit for constructing an "=" operator can be seen in Figure 1. A circuit labeled with wires can be seen in 2. To construct a garbled circuit, first each wire has to be assigned two random t bit strings. There are two strings to cover the 0 and 1 input cases. In an actual garbled circuit, t would be set to 80. For demonstrative purposes, t will be 8 in this case. Table 1 shows the random strings assigned to each wire where v_a^b such that a is the wire and b is the bit the string represents. Next, a permutation bit must be randomly chosen for each wire. This can be found in Table 2. The random permutation is appended to v_i^j to form w_i^j such that $w_k^0 = v_k^0 || (0 \oplus p_k)$ and $w_k^1 = v_k^1 || (1 \oplus p_k)$. Each w_i^j value can be seen in Table 3.

Following this, each truth table is replaced with its corresponding Garbled-Truth-Table (GTT) by replacing each 0 or 1 with w_k^0 or w_k^1 respectively. The GTT is replaced by the Encrypted-Garbled-Truth-Table (EGTT) which is an encrypted version of the GTT. The encryption is performed by SHA1 hashing $v_i^x || k || x' || y'$ with the plane text w_k^x where $x' = x \oplus p_i$ and $y' = y \oplus p_j$ and x, y are the entries in the original truth table. This encryption will be represented as $Enc(w_i^j)$.

To make the Permuted-Encrypted-Garbled-Truth-Table (PEGTT), the rows in the EGTT have to be swapped based on the following rule: if $p_i = 1$, the first two entries of the table are swapped with the last two entries; if $p_j = 1$, then the first and third are swapped and the second and fourth entries are swapped. The GTT, EGTT, and PEGTT for gate 0 can be found in Table 4.

Figure 1: Normal Circuit

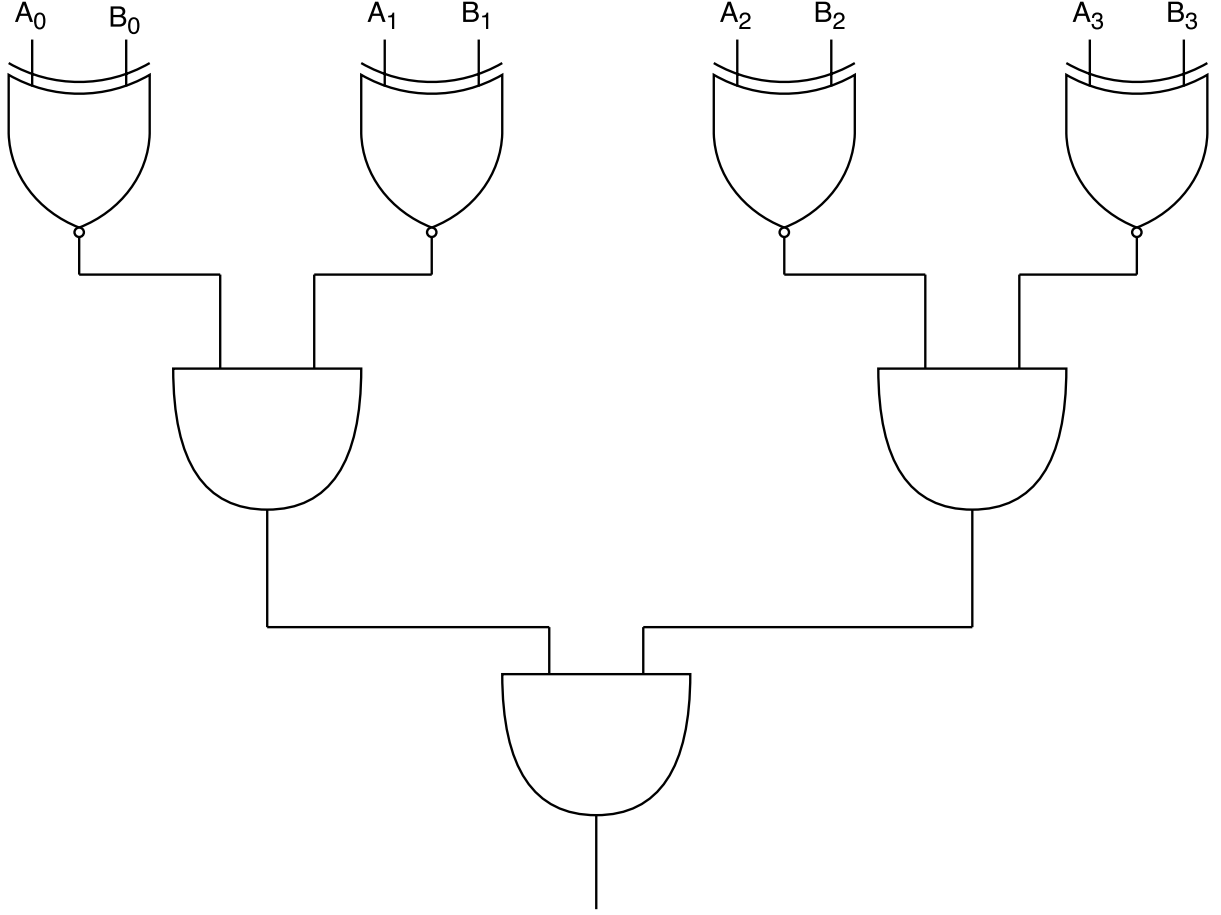


Table 1: Random t-bit Strings

| | |
|-----------------------|-----------------------|
| $v_0^0 = 00000000$ | $v_0^1 = 11111111$ |
| $v_1^0 = 00000001$ | $v_1^1 = 10000000$ |
| $v_2^0 = 00000010$ | $v_2^1 = 01000000$ |
| $v_3^0 = 00000011$ | $v_3^1 = 11000000$ |
| $v_4^0 = 00000100$ | $v_4^1 = 00100000$ |
| $v_5^0 = 00000101$ | $v_5^1 = 10100000$ |
| $v_6^0 = 00000110$ | $v_6^1 = 01100000$ |
| $v_7^0 = 00000111$ | $v_7^1 = 11100000$ |
| $v_8^0 = 00001000$ | $v_8^1 = 00010000$ |
| $v_9^0 = 00001001$ | $v_9^1 = 10010000$ |
| $v_{10}^0 = 00001010$ | $v_{10}^1 = 01010000$ |
| $v_{11}^0 = 00001011$ | $v_{11}^1 = 11010000$ |
| $v_{12}^0 = 00001100$ | $v_{12}^1 = 00110000$ |
| $v_{13}^0 = 00001101$ | $v_{13}^1 = 10110000$ |
| $v_{14}^0 = 00001110$ | $v_{14}^1 = 01110000$ |

Figure 2: Garbled Circuit Wires

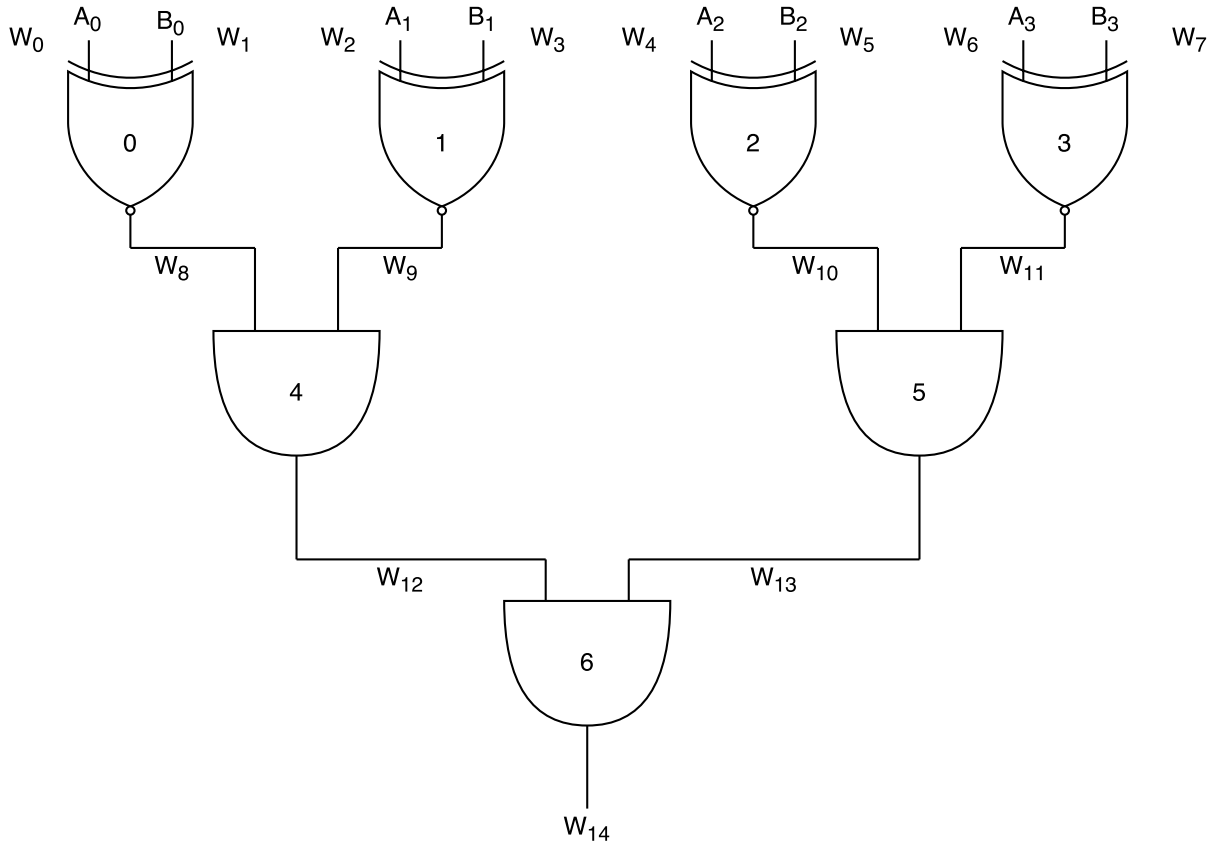


Table 2: Permutation Bit

| |
|--------------|
| $p_0 = 0$ |
| $p_1 = 1$ |
| $p_2 = 0$ |
| $p_3 = 1$ |
| $p_4 = 0$ |
| $p_5 = 1$ |
| $p_6 = 0$ |
| $p_7 = 1$ |
| $p_8 = 0$ |
| $p_9 = 1$ |
| $p_{10} = 0$ |
| $p_{11} = 1$ |
| $p_{12} = 0$ |
| $p_{13} = 1$ |
| $p_{14} = 0$ |

Table 3: Wire Strings

| | |
|------------------------|------------------------|
| $w_0^0 = 000000000$ | $w_0^1 = 111111111$ |
| $w_1^0 = 000000011$ | $w_1^1 = 100000000$ |
| $w_2^0 = 000000100$ | $w_2^1 = 010000001$ |
| $w_3^0 = 000000111$ | $w_3^1 = 110000000$ |
| $w_4^0 = 000001000$ | $w_4^1 = 001000001$ |
| $w_5^0 = 000001011$ | $w_5^1 = 101000000$ |
| $w_6^0 = 000001100$ | $w_6^1 = 011000001$ |
| $w_7^0 = 000001111$ | $w_7^1 = 111000000$ |
| $w_8^0 = 000010000$ | $w_8^1 = 000100001$ |
| $w_9^0 = 000010011$ | $w_9^1 = 100100000$ |
| $w_{10}^0 = 000010100$ | $w_{10}^1 = 010100001$ |
| $w_{11}^0 = 000010111$ | $w_{11}^1 = 110100000$ |
| $w_{12}^0 = 000011000$ | $w_{12}^1 = 001100001$ |
| $w_{13}^0 = 000011011$ | $w_{13}^1 = 101100000$ |
| $w_{14}^0 = 000011100$ | $w_{14}^1 = 011100001$ |

Table 4: GTT, EGTT, PEGTT for Gate 0

| Truth Table | | | GTT | | | EGTT | | | PEGTT | | |
|-------------|---|-----|---------|---------|---------|--------------|--------------|--------------|--------------|--------------|--------------|
| X | Y | Out | X | Y | Out | X | Y | Out | X | Y | Out |
| 0 | 0 | 1 | w_0^0 | w_1^0 | w_8^1 | $Enc(w_0^0)$ | $Enc(w_1^0)$ | $Enc(w_8^1)$ | $Enc(w_0^0)$ | $Enc(w_1^0)$ | $Enc(w_8^1)$ |